



Table of Contents

Chapter 5 Alternating Current

Unit 16 Alternating Current 195

Introduction..... 195

16.1 Current Flow 195

16.2 Why Alternating Current is Used 195

16.3 How Alternating Current is Produced 196

16.4 AC Generator 196

16.5 Waveform 197

Direct-Current Waveform 197

Alternating-Current Waveform 197

16.6 Sine Wave 197

Sinusoidal Waveform 197

Nonsinusoidal Waveform..... 198

16.7 Nonsymmetrical Waveform 198

16.8 Frequency 198

16.9 Phase..... 198

16.10 Degrees 198

16.11 Lead or Lag 199

Leading..... 199

Lagging..... 199

16.12 Values of Alternating Current 199

Instantaneous 199

Peak..... 199

RMS 200

Unit 16 – Summary 201

Unit 16 – Conclusion 202

Unit 16 – Practice Questions 203

Unit 17 Capacitance 207

Introduction..... 207

Capacitor Current Flow 207

17.1 Charged Capacitor 207

17.2 Electrical Field..... 208

17.3 Discharging a Capacitor..... 208

17.4 Determining Capacitance..... 208

Plate Distance..... 208

Surface Area 208

Dielectric Strength 209

17.5 Uses of Capacitors 209

Electronic Power Supplies..... 209

17.6 Phase Relationship 209

Unit 17 – Summary 211

Unit 17 – Conclusion 212

Unit 17 – Practice Questions 213

Unit 18 Induction 215

Introduction..... 215

18.1 Self-Induction 215

18.2 Induced Voltage and Applied Current 216

Opposes Current Flow 216

Aids the Current Flow 216

18.3 Conductor AC Resistance..... 216

Eddy Currents 217

Skin Effect 217

18.4 Impedance 217

18.5 Conductor Shape 217

Current..... 217

Winding..... 218

Frequency 218

18.6 Magnetic Cores..... 218

Core Material 218

Core Length 218

Core Area 218

18.7 Self-Induced and Applied Voltage 218

18.8 Current Flow 219

Inductive Reactance..... 219

18.9 Phase Relationship 219

18.10 Uses of Induction 219

Unit 18 – Summary 220

Unit 18 – Conclusion 221

Unit 18 – Practice Questions 222

Unit 19 Power Factor and Efficiency 227

Introduction..... 227

Inductors and Capacitors 227

Part A – Power Factor 227

19.1 Apparent Power (Volt-Ampere)..... 227

19.2	True Power (Watts).....	228	Squirrel-Cage Induction Motor	251
	Direct Current	228	Synchronous Motor	251
	Alternating Current.....	228	Wound-Rotor Motor	251
19.3	Power Factor.....	228	Universal Motor.....	252
19.4	Unity Power Factor.....	228	20.15 Reversing the Rotation of an AC Motor	252
19.5	Power Factor Formulas	229	Unit 20 – Summary	253
19.6	Cost of True Power.....	229	Unit 20 – Conclusion	255
19.7	Effects of Power Factor	230	Unit 20 – Practice Questions	256
Part B – Efficiency	231	Unit 21 Generators	259	
19.8	Efficiency	231	Introduction.....	259
19.9	Efficiency Formulas.....	232	21.1 Direct-Current Generator	259
Unit 19 – Summary	234	Excitation Current	259	
Unit 19 – Conclusion	235	21.2 Alternating-Current Generator.....	260	
Unit 19 – Practice Questions	236	21.3 Three-Phase Generators	260	
Chapter 5 Final Review Questions	239	21.4 Voltage Phase Relationship.....	261	
Chapter 6		Unit 21 – Summary	262	
Motors, Generators and Transformers		Unit 21 – Conclusion	262	
Unit 20 Motors	245	Unit 21 – Practice Questions	263	
Introduction.....	245	Unit 22 Transformers	265	
Part A – Motor Basics	245	Introduction	265	
20.1 Motor Principles.....	245	22.1 Transformer Basics	265	
Stator.....	245	Primary Versus Secondary	265	
Rotor.....	245	Mutual Induction	265	
20.2 Dual-Voltage AC Motors.....	245	22.2 Secondary Induced Voltage.....	265	
20.3 Motor Horsepower Rating	245	22.3 Autotransformers	266	
20.4 Motor Current Ratings.....	246	Step Down.....	266	
Motor Full-Load Ampere (FLA) Rating	246	Step Up.....	266	
Actual Motor Current.....	246	22.4 Power Losses	267	
Motor Full-Load Current Rating (FLC)	247	Conductor Resistance Loss.....	267	
20.5 Calculating Motor FLA.....	247	Flux Leakage Loss	267	
Single-Phase.....	247	Eddy Currents	267	
3-Phase	247	Hysteresis Losses	268	
20.6 Motor-Starting Current	248	22.5 Harmonic Current	268	
20.7 Motor-Running Current	248	22.6 Efficiency	269	
20.8 Motor Locked Rotor Current (LRC)	249	22.7 Transformer Turns' Ratio.....	269	
20.9 Motor Overload Protection	249	22.8 Transformer kVA Rating	270	
NEC Requirement.....	249	22.9 Current Flow	270	
Part B – Direct-Current Motors	250	22.10 Current Rating	271	
20.10 Direct-Current Motor Principles	250	Unit 22 – Summary	273	
20.11 Direct-Current Types.....	250	Unit 22 – Conclusion	274	
Shunt-Wound DC Motor	250	Unit 22 - Practice Questions.....	275	
Series-Wound DC Motor	250	Chapter 6 – Final Review Questions	277	
20.12 Reversing the Rotation of a DC Motor	250			
Part C – Alternating-Current Motors	250			
20.13 AC Induction Motor	250			
20.14 Alternating-Current Motor Types.....	251			