

# Contents

## CHAPTER 1 ELECTRICAL FUNDAMENTALS

### *Unit 1 Matter*

1-1	Introduction.....	1
1-2	Law of Electric Charges.....	3
1-3	Atomic Charges.....	4
1-4	Charged Material.....	4
1-5	Charged Material (Static Electricity).....	5
1-6	Neutralizing a Charge.....	6
Unit 1	Summary.....	8
Unit 1	Questions.....	9

### *Unit 2 Electron Theory*

2-1	Electron Orbits.....	11
2-2	Outer (Valance) Shell.....	11
2-3	Freeing Electron.....	11
2-4	Conductors.....	12
2-5	Insulators.....	12
2-6	Semiconductor.....	12
2-7	Atomic Bonding.....	12
Unit 2	Summary.....	14
Unit 2	Questions.....	15

### *Unit 3 Electricity*

3-1	Static Electricity.....	17
3-2	Electrical Current.....	18
3-3	Purpose Of Electricity.....	21
3-4	How Electricity Is Produced.....	23
3-5	How Electricity Is Used.....	24
Unit 3	Summary.....	25
Unit 3	Questions.....	27

### *Unit 4 Magnetism*

Introduction.....	29	
4-1	The Natural Magnet.....	29
4-2	Magnetic Polarities.....	29
4-3	Magnetic Compass.....	30
4-4	Magnetic Molecule.....	30
4-5	Magnetic Materials.....	30
4-6	How To Magnetize Iron.....	30
4-7	Permanent And Temporary Magnet.....	30
4-8	Demagnetizing A Magnet.....	31
4-9	Lines Of Force.....	31
4-10	Magnetic Materials.....	31
4-11	Law Of Attraction And Repulsion.....	31
4-12	Retentivity.....	31
4-13	Permeability.....	31
Unit 4	Summary.....	32
Unit 4	Questions.....	34

### *Unit 5 Electro-Magnetism*

5-1	Electromagnetism In A Wire.....	37
5-2	Field Intensity.....	37
5-3	Field Interaction.....	38
5-4	Field of Interaction Of Loops.....	38
5-5	Electromagnetism In A Coil.....	38
5-7	Magnetic Core.....	39
Unit 5	Summary.....	40
Unit 5	Questions.....	41

### *Unit 6 Uses Of Magnetism*

6-1	Basic Electric Meters.....	43
6-2	Electric Motor.....	46
6-3	Electric Generator.....	48
6-4	Electromagnetic Relay.....	49

6-5	Holding Relay .....	50
Unit 6	Questions .....	51

## CHAPTER 2 OHM'S LAW & SERIES CIRCUITS

### *Unit 7 The Electrical Circuit*

7-1	The Electrical Circuit .....	55
7-2	Voltage .....	55
7-3	Resistance .....	56
7-4	Current .....	56
7-5	Power .....	57
7-6	Formulas .....	57
Unit 7	Summary .....	59
Unit 7	Questions .....	60

### *Unit 8 Math*

Introduction.....	63	
8-1	Whole Numbers .....	63
8-2	Decimals .....	63
8-3	Fractions .....	63
8-4	Percentages .....	64
8-5	Multiplier .....	64
8-6	Percent Increase .....	65
8-7	Percentage Reciprocals .....	66
8-8	Squaring .....	66
8-9	Square Root .....	68
8-10	Cubic .....	68
8-11	Kilo .....	69
8-12	Rounding Off .....	69
8-13	Parentheses .....	70
8-14	Transposing Formulas .....	71
8-15	Knowing Your Answer .....	71
Unit 8	Summary .....	73
Unit 8	Questions .....	75

### *Unit 9 Electrical Formulas*

9-1	Electrical Circuits .....	79
9-2	Electron Flow .....	79
9-3	Power Source .....	80
9-4	Conductance .....	80
9-5	Circuit Resistance .....	81
9-6	Ohm's Law .....	81
9-7	Ohm's Law And Alternating Current .....	82
9-8	Ohm's Law Circle .....	82
9-9	Pie Circle .....	84

9-10	Power Wheel .....	86
9-11	Using The Power Wheel .....	86
9-12	Power Losses Of Conductors .....	88
9-13	Cost Of Power Loss .....	89
9-14	Power Changes With The Square Of The Voltage .....	90
Unit 9	Summary .....	93
Unit 9	Questions .....	95

## CHAPTER 3 SERIES-PARALLEL & MULTIWIRED CIRCUITS

### *Unit 10 Series Circuits*

Introduction.....	101	
10-1	Practical Uses .....	101
10-2	Understanding Series Calculations .....	103
10-3	Steps For Series Circuits .....	106
10-4	Voltage Drop Calculations .....	106
10-5	Power Calculations .....	107
10-6	Variations .....	107
10-7	Series Circuit Notes .....	107
10-8	Series Connected Power Supplies .....	107
Unit 10	Summary .....	109
Unit 10	Questions .....	111

### *Unit 11 Parallel Circuits*

Introduction.....	113	
11-1	Practical Uses .....	114
11-2	Understanding Parallel Calculations .....	114
11-3	Circuit Resistance .....	117
11-4	Variations .....	119
11-5	Parallel Circuit Notes .....	119
11-6	Parallel Connected Power Supplies .....	119
Unit 11	Summary .....	121
Unit 11	Questions .....	122

### *Unit 12 Series-Parallel Circuits*

Introduction.....	125	
12-1	Review Of Series And Parallel Circuits .....	125
12-2	Working of Series-Parallel Circuits .....	126
12-3	Voltage .....	127
12-4	Current .....	128
12-5	Power .....	129
Unit 12	Summary .....	130
Unit 12	Questions .....	131

**Unit 13 Multiwire Circuits**

Introduction.....	133
13-1 Neutral Conductor.....	133
13-2 Grounded Conductor.....	133
13-3 Current Flow On The Grounded Conductor....	135
13-4 Balanced Systems.....	135
13-5 Unbalanced Current.....	135
13-6 Sizing Of The Grounded Conductor.....	137
13-7 Multiwire Branch Circuit.....	137
13-8 Dangers of Multiwire Circuits.....	138
13-9 Why Multiwire Circuits Are So Dangerous.....	138
13-10 NEC Code Requirements.....	140
13-11 Another Disadvantage of Multiwire Circuits..	140
Unit 13 Summary.....	141
Unit 13 Questions.....	143

**CHAPTER 4  
A-C CIRCUITS & EQUIPMENT****Unit 14 The Electrical System**

Introduction.....	149
14-1 The Generating Plant.....	150
14-2 Step-Up Substations.....	151
14-3 Transmission Lines.....	151
14-4 Step-Down Substations.....	151
14-5 Primary Distribution Lines.....	152
14-6 Distribution Transformers.....	152
14-7 Secondary Distribution Lines.....	152
14-8 Customer Service.....	152
Unit 14 Summary.....	153
Unit 14 Questions.....	154

**Unit 15 Circuit Protection & Fault Hazards**

15-1 Overcurrent Protection.....	155
15-2 Clearing Fault Currents.....	155
15-3 Interrupting Rating.....	157
15-4 Withstand Rating.....	157
15-5 Current Limiting.....	157
15-6 Purpose of Grounding.....	158
15-7 Clearing Ground Faults.....	158
15-8 Hazards of Energized Parts.....	159
Unit 15 Summary.....	161
Unit 15 Questions.....	163

**Unit 16 Alternating Current**

16-1 Current Flow.....	167
------------------------	-----

16-2 Why Alternating Current Is Used.....	167
16-3 How Alternating Current Is Produced.....	167
16-4 A-C Generator.....	168
16-5 Waveform.....	169
16-6 Sine Wave.....	169
16-7 Nonsymmetrical Waveform.....	170
16-8 Frequency.....	170
16-9 Phase.....	170
16-10 Degrees.....	170
16-11 Lead or Lag.....	170
16-12 Values Of Alternating Current.....	171
Unit 16 Summary.....	173
Unit 16 Questions.....	175

**Unit 17 Power Factor & Efficiency**

Introduction.....	177
17-1 Apparent Power.....	177
17-2 True Power (Watts).....	177
17-3 Power Factor.....	178
17-4 Unity Power Factor.....	179
17-5 Power Factor Formulas.....	179
17-6 Effects Of Power Factor.....	180
17-7 Efficiency.....	182
17-8 Efficiency Formulas.....	183
Unit 17 Summary.....	186
Unit 17 Questions.....	187

**Unit 18 Capacitance**

Introduction.....	191
18-1 Charged Capacitance.....	192
18-2 Electric Field.....	192
18-3 Discharging A Capacitor.....	192
18-4 Determining Capacitance.....	192
18-5 Uses Of Capacitors.....	193
18-6 Phase Relationship.....	194
Unit 18 Summary.....	195
Unit 18 Questions.....	196

**CHAPTER 5  
USES OF INDUCTION****Unit 19 Induction**

Introduction.....	199
19-1 Self-Induction.....	199
19-2 Induced Voltage And Applied Current.....	200
19-3 Conductor Impedance.....	200

19-4	Conductor Shape .....	201		
19-5	Magnetic Core .....	202		
19-6	Induced And Applied voltage.....	202		
19-7	Current Flow .....	203		
19-8	Phase Relationship .....	203		
19-9	Uses Of Self-Induction .....	204		
Unit 19	Summary .....	205		
Unit 19	Questions.....	207		
<b>Unit 20 Motors</b>				
	Introduction.....	211		
20-1	Speed Control .....	212		
20-2	Reversing A D-C Motor .....	212		
20-3	A-C Motors .....	212		
20-4	Reversing A-C Motors .....	213		
20-5	Dual Voltage Motors.....	214		
20-6	Motor Horsepower J Watts .....	214		
20-7	Motor Nameplate Amperes .....	216		
20-8	Motor Nameplate Formula .....	217		
20-9	Motor Overload .....	218		
20-10	Motor Starting current .....	219		
Unit 20	Summary .....	221		
Unit 20	Questions.....	222		
<b>Unit 21 Generators</b>				
21-1	Direct Current Generator .....	225		
21-2	Excitation Current .....	225		
21-3	Alternating Current Generator .....	225		
21-4	Three-phase Generators .....	226		
21-5	Delta Connected Armature Leads .....	227		
21-6	Wye Connected Armature Lead .....	228		
Unit 21	Summary .....	230		
Unit 22	Questions.....	231		
<b>Unit 22 Basic Transformers</b>				
	Introduction.....	235		
22-1	Primary vs. Secondary .....	236		
22-2	Secondary voltage .....	236		
22-3	Step-Up/Down Transformers.....	236		
22-4	Autotransformers .....	236		
22-5	Power Losses .....	237		
22-6	Efficiency .....	238		
22-7	Turns Ratio.....	129		
22-8	kVA Rating .....	240		
22-9	Transformer Current.....	240		
Unit 22	Summary .....	243		
Unit 22	Questions.....	245		